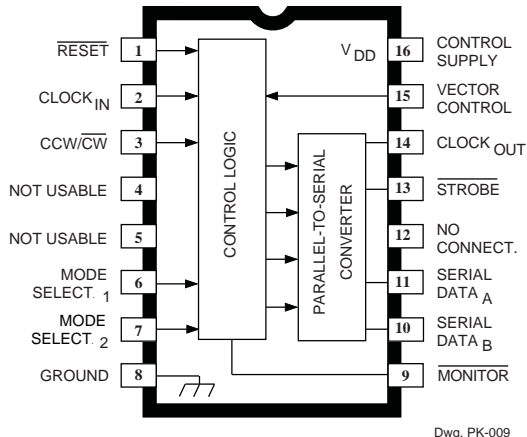


**PARALLEL-TO-SERIAL  
DATA CONVERTER****ABSOLUTE MAXIMUM RATINGS**

Supply Voltage, $V_{DD}$	7.0 V
Input Voltage Range, $V_I$	-0.5 V to $V_{DD} + 0.5$ V
Input Current, $I_I$	$\pm 10$ mA
Output Voltage Range, $V_O$	-0.5 V to $V_{DD} + 0.5$ V
Output Current, $I_O$	$\pm 15$ mA
Operating Temperature Range, $T_A$	-20°C to +85°C
Storage Temperature Range, $T_S$	-40°C to +150°C

*CAUTION: CMOS devices have input static protection but are susceptible to damage if exposed to extremely high static electrical charges.*

The PG001M CMOS IC converts parallel-data signals from a low-cost, 8-bit microprocessor or microcontroller into a serial-data format compatible with the SLA7042M and SLA7044M power multi-chip modules to drive unipolar PWM, high-current stepper motors. The converter provides for five basic modes of operation:

- 1) normal, two-phase, full step (100% torque vector),
- 2) two-phase 'boosted' torque (141% torque vector),
- 3) half-step, constant torque operation (using a 2-1-2 output switching),
- 4) quarter-stepping utilizing ratioed currents for constant torque, and
- 5) microstepping (1/8<sup>th</sup> steps) for quiet, smooth, resonance-free motor performance.

The PG001M is supplied in a low-cost 16-pin dual in-line plastic package. It is rated for continuous operation over the temperature range of -20°C to +85°C.

**FEATURES**

- Intended For Use With SLA7042M or SLA7044M Microstepping, Unipolar PWM, High-Current Motor Drivers
- Supports Five Stepper-Motor Operating Modes
- $\mu$ P-Compatible Inputs


Always order by complete part number, **PG001M**.

# PG001M

## PARALLEL-TO-SERIAL DATA CONVERTER

Integrated  
Circuits

### FUNCTIONAL BLOCK DIAGRAM

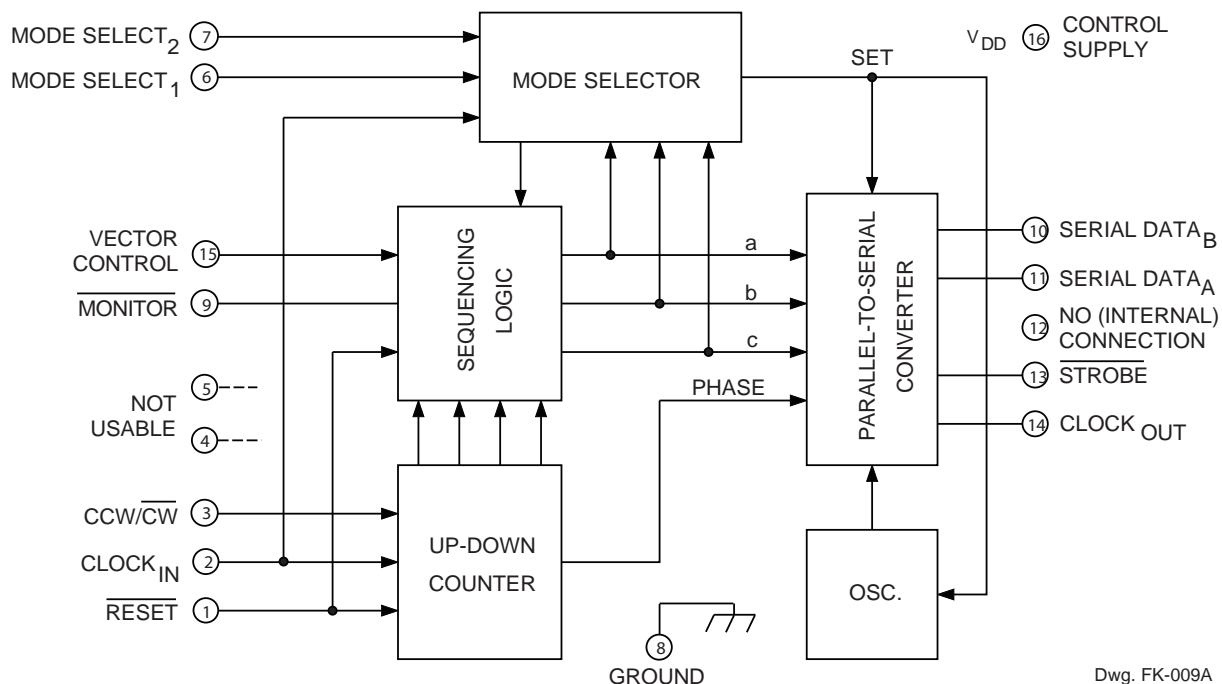


### TRUTH TABLE

Motor Excitation	PG001M Inputs			SLA7042/44M Output Sequence & PWM Current								Motor Torque
				0	1	2	3	4	5	6	7	
	VC	MS <sub>1</sub>	MS <sub>2</sub>	0%	20%	40%	55.5%	71.4%	83%	91%	100%	
Full Step	H	L	L	—	—	—	—	—	—	—	■	141%
	L	L	L	—	—	—	—	■	—	—	—	100%
Half Step	X	H	L	■	—	—	—	■	—	—	■	100%
1/4 Step	X	L	H	■	—	■	—	■	—	■	■	100%
1/8 Step	X	H	H	■	■	■	■	■	■	■	■	100%

This data sheet is based on Sanken data sheet SSJ-01367.

**ELECTRICAL CHARACTERISTICS at  $T_A = +25^\circ\text{C}$ ,  $V_{DD} = 5\text{ V}$  (unless otherwise noted).**

Characteristic	Symbol	Test Conditions	Limits			
			Min.	Typ.	Max.	Units
Supply Voltage	$V_{DD}$	Operating	4.5	—	5.5	V
Output Voltage	$V_{OH}$	$I_O = -3\text{ mA}$	4.5	4.6	—	V
	$V_{OL}$	$I_O = 3\text{ mA}$	—	0.3	0.4	V
Input Current	$I_{IH}$	$V_I = 5\text{ V}$	—	—	1.0	$\mu\text{A}$
	$I_{IL}$	$V_I = 0\text{ V}$	—	—	-1.0	$\mu\text{A}$
Input Voltage	$V_{IH}$		3.5	—	5.0	V
	$V_{IL}$		0	—	1.5	V
	$V_{hys}$		—	1.0	—	V
Internal Oscillator Freq.	$f_{osc}$		—	1.5	—	MHz
Delay Time	$t_{d(CIH-COH)}$	$\text{CLK}_{IN}$ to $\text{CLK}_{OUT}$ rising edges	—	50	100	ns
	$t_{d(CIL-SL)}$	$\text{CLK}_{IN}$ to STROBE falling edges	—	430	550	ns
Output Switching Time	$t_r$	$C_L = 15\text{ pF}$ , 10% to 90%	—	20	—	ns
	$t_f$	$C_L = 15\text{ pF}$ , 90% to 10%	—	20	—	ns
$\text{CLOCK}_{IN}$ Pulse Width	$t_{ckH}$		4.5	—	—	$\mu\text{s}$
	$t_{ckL}$		0.5	—	—	$\mu\text{s}$
Input Capacitance	$C_i$		—	5.0	10	pF
Supply Current	$I_{DD}$	$V_{DD} = 5.5\text{ V}$	—	350	450	$\mu\text{A}$

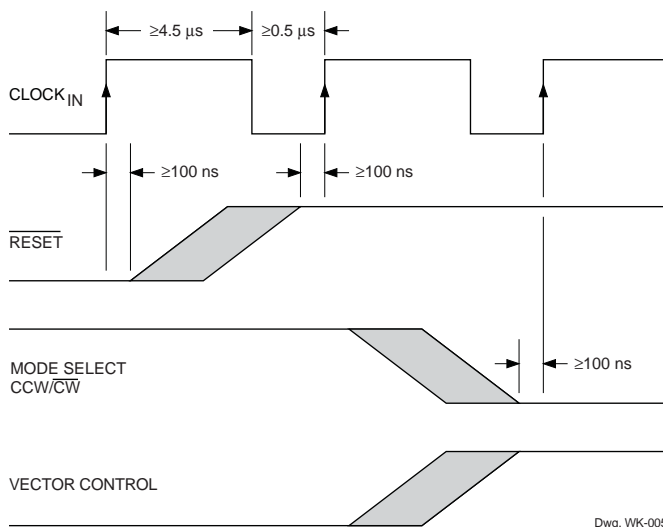


PG001M Input Signals Timing

Dwg. WK-005

# PG001M PARALLEL-TO-SERIAL DATA CONVERTER

Integrated  
Circuits

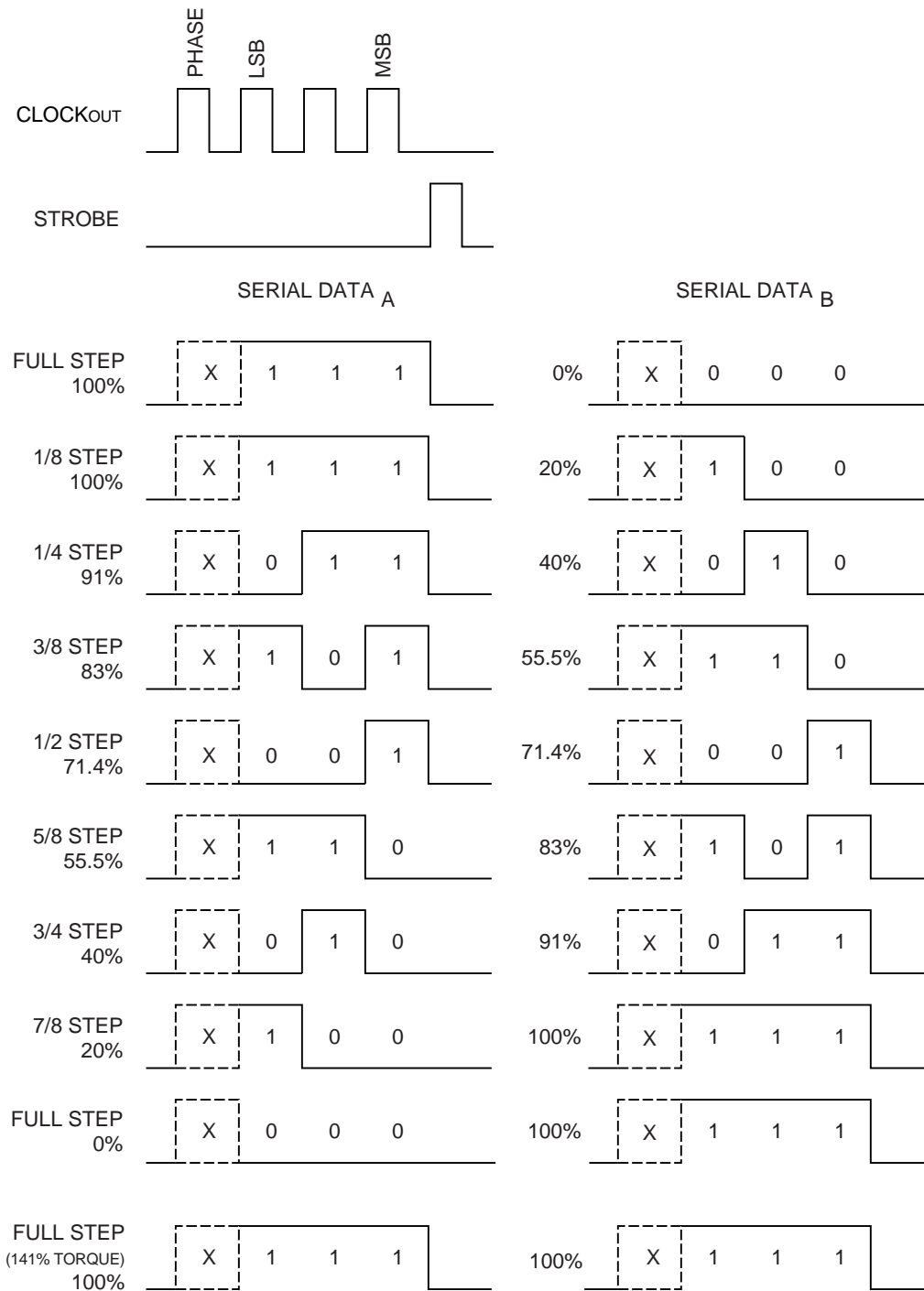

Dwg. WK-007

CLOCK, STROBE, and SERIAL DATA Outputs for Microstepping

## PG001M DESCRIPTION AND OPERATION

The PG001M is a CMOS step-motor control IC that converts parallel-input signals from a microprocessor ( $\mu P$ , or microcontroller,  $\mu C$ ) to the serial-input data format required for control of an SLA7042M or SLA7044M microstepping, unipolar PWM, high-current motor driver. This control IC offers five basic modes of motor operation:


- 1) normal 2-phase, full-step (100% torque vector);
- 2) 2-phase, full-step 'boosted' torque (141% vector);
- 3) 1/2-step, constant torque operation (i.e., 2-1-2 switching);
- 4) 1/4-step operation with current-ratioed constant torque; and
- 5) smooth microstepping operation (1/8<sup>th</sup> step) for resonance-free motor performance (constant torque with eight output current ratios).

Three inputs (VC, MS<sub>1</sub>, and MS<sub>2</sub>) control these five operational modes (as shown in figure 1); this enables designers to change the drive method during movement to realize optimal performance.

Initially, at start-up, the high-torque mode can provide 141% torque (the resulting vector of both motor windings at 100% current). This enhances rapid acceleration (and deceleration). Switching to quarter-stepping or microstepping (after initial, startup acceleration) offers smooth, resonance-free operation during the ramp-up interval. The transition to quarter- or microstepping should occur before the increasing step rate approaches the motor resonance frequency (usually 100 to 200 Hz).

The modes of operation and current-control truth table are listed on page 2; and there are two full-step, 2-phase (2-2) operating modes. The VECTOR CONTROL input (VC) can only be changed when MONITOR (MO, a readback pin) is LOW and the PG001M is operating in the full-step mode. Starting (or stopping) the step motor with VC HIGH delivers the highest torque (141%) from the motor, and is the extension of two outputs ON at 71.4%. This 'half-step' rotor position corresponds to the state when MO is LOW, and switching the control inputs to another operating mode is allowed.

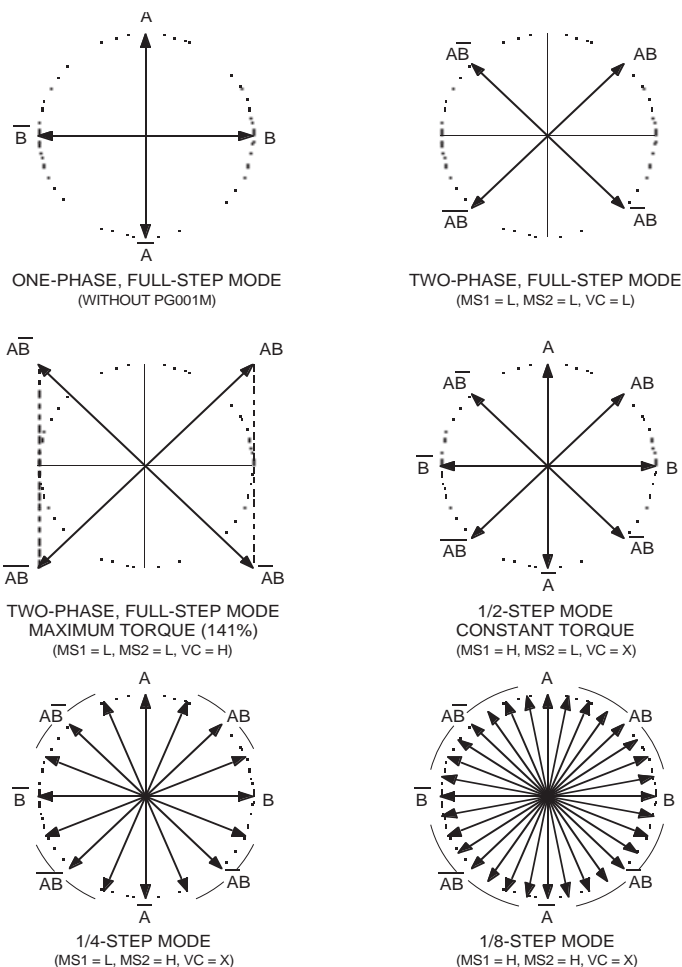The PG001M accepts logic signals from the  $\mu P$  and converts these into the proper serial-data format required to control the serial-data input lines of the SLA7042M or SLA7044M microstepping power modules. The five



Dwg. OP-005

NOTE – Mode change only allowed at half-step positions (refer to upper right figure).

Figure 1 — Current/Displacement Vectors

control inputs determine the various modes of operation. The CLOCK<sub>OUT</sub>, SERIAL DATA<sub>A</sub>, SERIAL DATA<sub>B</sub>, and STROBE to the SLA7042/44M are synchronized to the CLOCK<sub>IN</sub> of the PG001M; and the CLOCK<sub>IN</sub> frequency is eight times the step rate (more to follow on the signal/timing relationships).

The internal logic and oscillator combine to convert the parallel input signals to 'bursts' of serial data from the

# PG001M

## PARALLEL-TO-SERIAL DATA CONVERTER

Integrated  
Circuits

CLOCK<sub>OUT</sub>, SERIAL DATA<sub>A</sub>, SERIAL DATA<sub>B</sub>, and STROBE. In the full-step modes the clock, data, and strobe pulses are 1/8 the input clock rate; while half-step operation produces 'bursts' at 1/4 the input clock rate. Further, quarter-step mode signals correspond to 1/2 the input clock frequency; while during microstepping the signal 'bursts' equal the input clock rate. Hence, the step rate is always 1/8<sup>th</sup> the input clock frequency, regardless of the operating mode. Obviously, the clock rate increases while accelerating, becomes constant during slewing, and decreases as the step motor and load are decelerating.

### Microstepping Operation

Figures 1 and 2 illustrate the incremental eight step divisions provided while microstepping. The 3-bit sequence from 0 through 8 provides smooth, constant-torque operation that is delivered to the motor/load by the SLA7042M or SLA7044M power multi-chip modules.

The circle in figure 1 and the arc in figure 2 represent the constant-torque vectors. Slight discrepancies are evident when examining the vector 'arrows'. The disparity is insignificant, and will not affect smooth, resonance-free motion. However, it may affect realizing accurate and precise intermediate positioning. Subdividing steps into

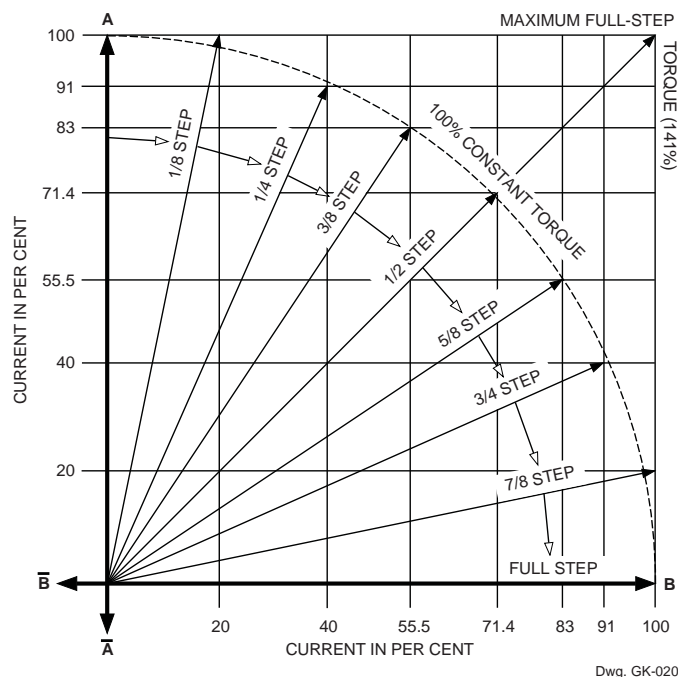


Figure 2 — Current/Displacement Vectors

eight distinct, exact positions is often very challenging. Clearly, variation in the phase currents affects rotor displacement, and is a very crucial factor in resolving accurate, intermediate step divisions.

Another critical factor to realizing precise, repeatable step subdivisions pertains to the selection and evaluation of the step motor. The better motors exhibit uniformly spaced positioning characteristics. However, torque vs displacement characteristics vary (often greatly). Usually, precise step subdivisions require motors designed for microstepping.

### An 'Integrated' Microstepping Design


The combination of CMOS controller IC and microstepping power module is depicted in figure 3. The  $\mu$ P provides the needed logic signals that reset the counter, control rotor direction, determine the operating mode, and change the current/torque vector (during full-step, 2-phase operation).

The sequencing logic provides a 'readback' signal (the MO output) that switches LOW at the half-step position when the microcontroller can shift control modes and not incur oscillation/vibration problems. The mode change is allowed at the 45° vector, half-step position shown in figure 2. In addition to the 45° AB vector, three other half-step vectors occur during stepping: AB at 135°, AB at 225°, and AB at 315° (figure 1). These current vectors correspond to the half-step positions in four quadrants, and four 2-phase, full steps of rotation.
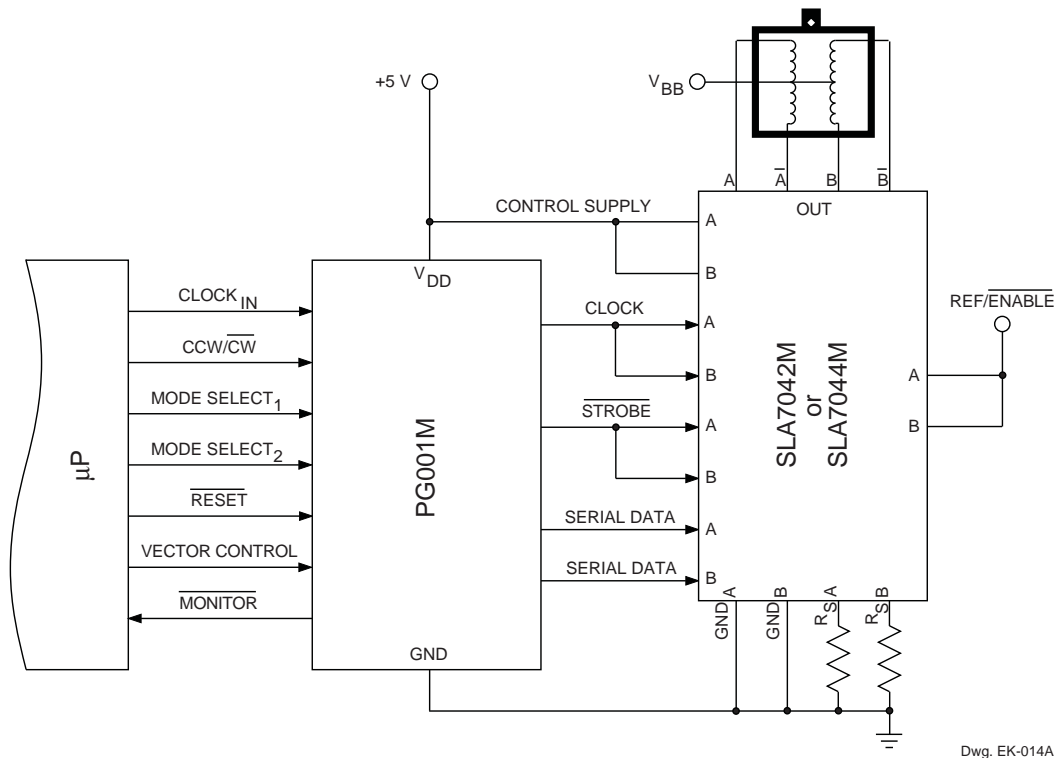
### The Parallel-to-Serial Conversion

Perhaps the greatest system advantage for designers is the simplification of software. Controlling and operating the SLA7042/44M power multi-chip modules directly would require programming the system  $\mu$ P to provide and update serial data to both the A and B inputs, and signals to the clock and strobe inputs that control the A and B sections of the driver.

Although designs utilizing the CMOS control IC require seven I/O lines, the software program will be simpler and shorter. The system  $\mu$ P provides logic signals that control RESET, CCW/CW (direction), MODE SELECT<sub>1</sub>, MODE SELECT<sub>2</sub>, VECTOR CONTROL, and read the MONITOR return. Only the CLOCK input is a 'dynamic', constantly switching signal from the system control I/O.



Dwg. EK-014A

Figure 3 — Typical 'Integrated' Microstepping System

Depicted in figure 4 are the 'front-end' I/O signals (from RESET to VECTOR CONTROL), converted signals from the controller IC to the microstepping power module (CLOCK<sub>OUT</sub>, SERIAL DATA<sub>A</sub>, SERIAL DATA<sub>B</sub>, and STROBE), plus the MONITOR (readback) to the microcontroller. Finally, the power multi-chip module current ratios are illustrated (OUT<sub>A</sub> and OUT<sub>B</sub>).

As shown, initially the counter is reset, and then the motor is operating in quarter-step mode; then MS<sub>2</sub> is switched while MO is LOW. The two steps following are full-step (100% torque vector). The final (fourth quadrant) portion of figure 4 is the maximum (141%) torque mode, after VECTOR CONTROL has been switched from LOW to HIGH. Three of the five operational modes are shown, and none require the μP to continually update the clock, serial-data input, or strobe to the SLA7042/44M module.

The microstepping operation is illustrated in figure 5. Initially the counter is reset, and with both MODE SELECTs HIGH the controller is furnishing clock, serial data, and strobe logic signals for 1/8<sup>th</sup> step increments.


After the RESET pulse, the first (two) full-steps in the microstepping sequence, MS<sub>1</sub> is switched LOW and the control IC shifts into the 1/4-step mode. It becomes very apparent that any microstepping directly from a μP to the SLA7042/44M module 'burdens' the μP, complicates the software, and might entail a 'dedicated' microcontroller in many motion-control systems.

The PG001M controller IC precludes loading a μP with direct serial-data signals to the power multi-chip module. Because the step motor is updated at eight times the step rate, this CMOS IC both simplifies software and eliminates loading a system microprocessor with 'house-keeping' control of step motors.

As illustrated in figures 4 and 5, the controller IC eliminates the requirement to program the system for the various modes of operation and the continual updating of the serial-data signals to the power multi-chip module. NOTE — In figures 4 and 5, the clock frequency is constant during the few steps of operation that are shown and half-step operation is not included.

# PG001M PARALLEL-TO-SERIAL DATA CONVERTER

Integrated  
Circuits

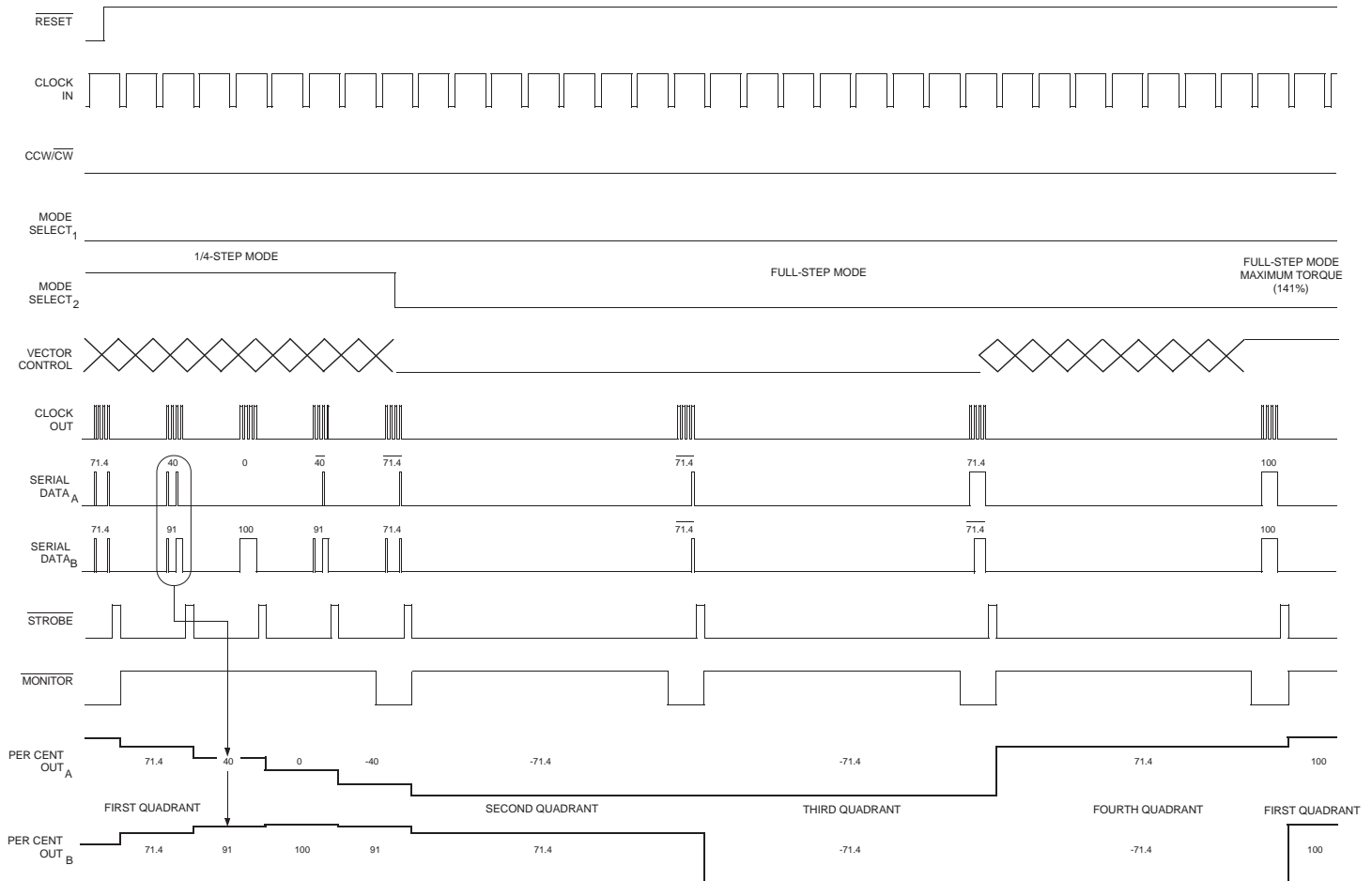


Dwg. WK-006

Figure 4 — Quarter-Step, Full-Step, and High-Torque Full-Step

Because the parallel-to-serial conversion requires six 'static' logic signals plus a 'dynamic' (clock) input, the addition of latches between the  $\mu$ P and five of the controller IC inputs permits use on a bus. Latching the five signals to CCW/CW,  $MS_1$ ,  $MS_2$ , RESET, and VC frees these five I/O lines for other operations by the microcontroller. Even at extremely high step rates ( $>5$  kHz), updating the PG001M input data requires an infinitesimal percentage of the  $\mu$ P's I/O and control operations.



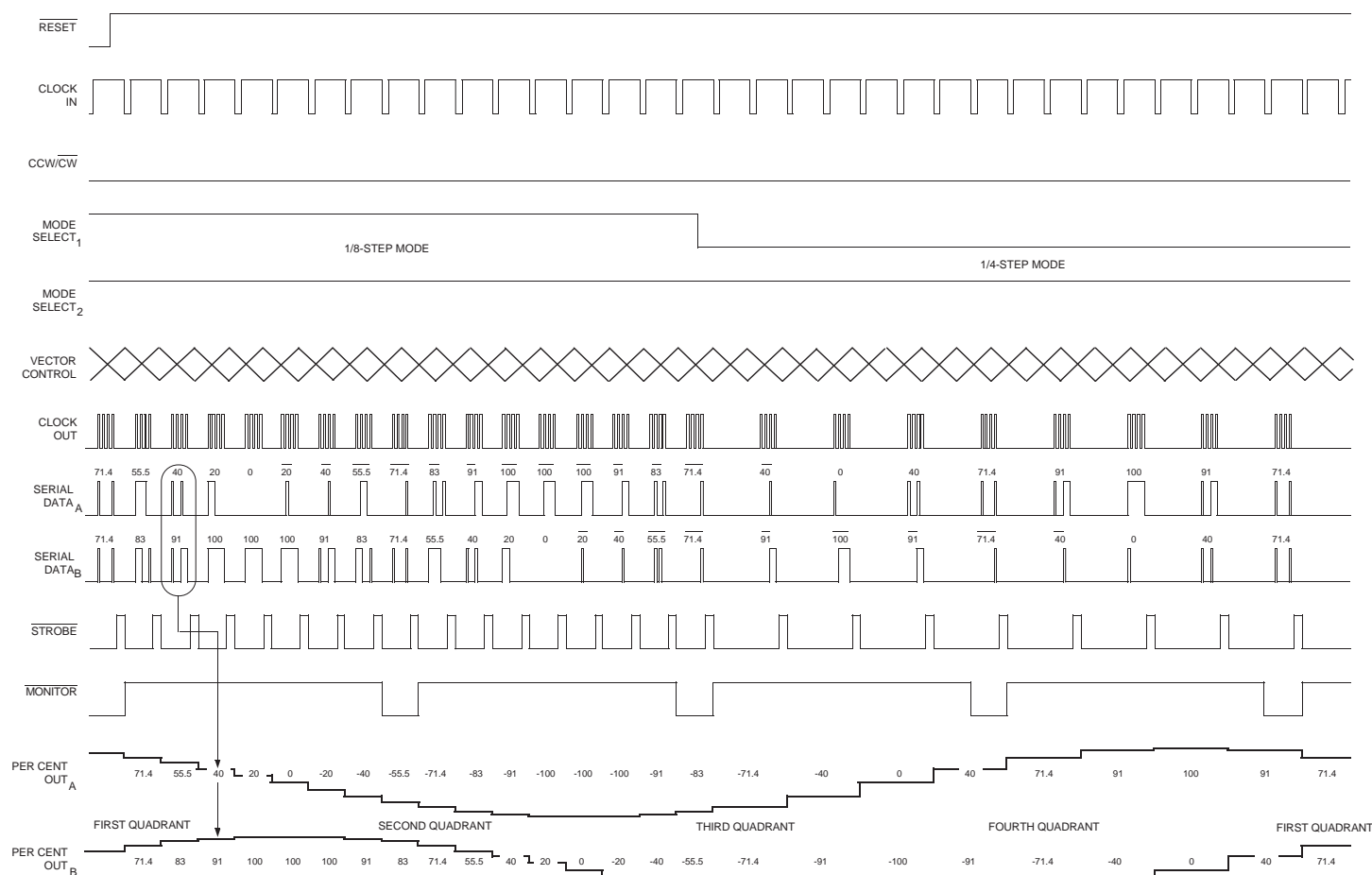

Dwg. WK-006-1

Figure 5 — Microstepping (1/8<sup>th</sup>-Step) and Quarter-Step Modes

One technique to free  $\mu\text{P}$  I/O lines for shared functions is depicted in figure 6. The I/O lines required (without latches) are then transformed into three 'dedicated' logic inputs; a STROBE is added, and CLOCK and MONITOR retained. CLOCK, RESET, MODE SELECT<sub>1</sub>, MODE SELECT<sub>2</sub>, and VECTOR CONTROL now connect to a bus.

The clock input frequency limit is derived from the figure on page 3. The minimum period for the clock pulse HIGH is 4.5  $\mu\text{s}$ , plus a minimum LOW interval of 0.5  $\mu\text{s}$ ; this limits the upper clock frequency to  $\leq 200$  kHz. Updating the operating mode of the controller IC requires only one clock period ( $\geq 5$   $\mu\text{s}$ ), and the five I/O lines on the bus remain unchanged until a signal is required to change the operating mode, reverse direction, vary torque, etc.

# PG001M PARALLEL-TO-SERIAL DATA CONVERTER

Integrated  
Circuits

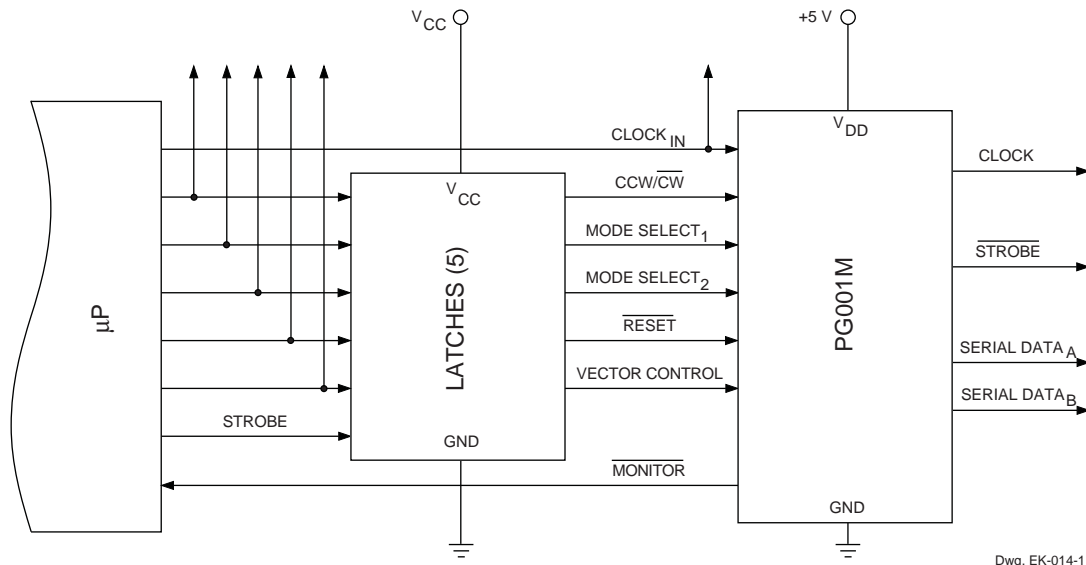


Figure 6 — A Latched Input-Bus Configuration

At start-up, resetting the counter adds only another clock interval (per figures 4 and 5). During high-speed slewing, the  $\mu$ P is only occupied with sending clock signals and monitoring the readback (MO). Hence, of a 200  $\mu$ s interval, with a slewing rate of 5 kHz, only 5  $\mu$ s is required to provide the clock input. At slower, more typical step rates, 5  $\mu$ s becomes an insignificant burden on the  $\mu$ P controlling the stepping motor.

Other techniques to decrease and unburden the essential  $\mu$ P I/O lines and control logic are viable. Utilizing an 8-bit shift register (serial-to-parallel conversion) between the  $\mu$ P and the controller IC further reduces the I/O lines, and HCMOS logic provides serial-data entry at 20 MHz (vs <200 kHz). Such a design could further decrease the interval required to update the step-motor operation and reduce the I/O lines on the bus.

0.280  
0.240

16

9

0.070  
0.045

0.775  
0.735

0.100  
BSC

8

0.005  
MIN

0.210  
MAX

0.015  
MIN

0.150  
0.115

0.022  
0.014

0.014  
0.008

0.430  
MAX

0.300  
BSC

Dwg. MA-001-16A in

[illegible]

- 11

# **PG001M**

## ***PARALLEL-TO-SERIAL DATA CONVERTER***

Integrated  
Circuits

- 
- The contents in this document are subject to changes, for improvement and other purposes, without notice. Make sure that this is the latest revision of the document before use.
  - Application and operation examples described in this document are quoted for the sole purpose of reference for the use of the products herein and Sanken can assume no responsibility for any infringement of industrial property rights, intellectual property rights or any other rights of Sanken or any third party which may result from its use.
  - Although Sanken undertakes to enhance the quality and reliability of its products, the occurrence of failure and defect of semiconductor products at a certain rate is inevitable. Users of Sanken products are requested to take, at their own risk, preventative measures including safety design of the equipment or systems against any possible injury, death, fires or damages to the society due to device failure or malfunction.
  - Sanken products listed in this document are designed and intended for the use as components in general purpose electronic equipment or apparatus (home appliances, office equipment, telecommunication equipment, measuring equipment, etc.).

When considering the use of Sanken products in the applications where higher reliability is required (transportation equipment and its control systems, traffic signal control systems or equipment, fire/crime alarm systems, various safety devices, etc.), and whenever long life expectancy is required even in general purpose electronic equipment or apparatus, please contact your nearest Sanken sales representative to discuss, prior to the use of the products herein.

The use of Sanken products without the written consent of Sanken in the applications where extremely high reliability is required (aerospace equipment, nuclear power control systems, life support systems, etc.) is strictly prohibited.

- In the case that you use Sanken products or design your products by using Sanken products, the reliability largely depends on the degree of derating to be made to the rated values. Derating may be interpreted as a case that an operation range is set by derating the load from each rated value or surge voltage or noise is considered for derating in order to assure or improve the reliability. In general, derating factors include electric stresses such as electric voltage, electric current, electric power etc., environmental stresses such as ambient temperature, humidity etc. and thermal stress caused due to self-heating of semiconductor products. For these stresses, instantaneous values, maximum values and minimum values must be taken into consideration.

In addition, it should be noted that since power devices or IC's including power devices have large self-heating value, the degree of derating of junction temperature affects the reliability significantly.

- When using the products specified herein by either (i) combining other products or materials therewith or (ii) physically, chemically or otherwise processing or treating the products, please duly consider all possible risks that may result from all such uses in advance and proceed therewith at your own responsibility.
  - Anti radioactive ray design is not considered for the products listed herein.
  - Sanken assumes no responsibility for any troubles, such as dropping products caused during transportation out of Sanken's distribution network.
  - The contents in this document must not be transcribed or copied without Sanken's written consent.
-